

Design of 8-bit Signed Pipelined Carry Save Multiplier

Course Project: EE5311 Digital IC Design

Arjun Menon V Srinivas R Ashwanth S
EE18B104 EE18B136 EE18B040
Electrical Engineering
IIT Madras

August- November, 2021

The drive folder containing the libraries for the designs can be accessed using this [link](#).

1 Summary

| SUMMARY | |
|---|-------------------------------------|
| Maximum Operating Frequency (w/o pipelining) | 2.062 GHz(RC extracted = 1.64 GHz) |
| Maximum Operating Frequency (with pipelining) | 3.704 GHz(RC extracted = 2.618 GHz) |
| Area of Layout | 111.251 μm^2 (L*W=919,432) |
| Aspect Ratio | 1:5.50 |

Table 1: Summary of Carry Save Multiplier characteristics

| FUNCTIONAL SIMULATION RESULTS | | |
|-------------------------------|------------------|------------------------------|
| X | Y | Z |
| 0000 1001 (9) | 0000 1111 (15) | 0000 0000 1000 0111 (135) |
| 1111 0110 (-10) | 0000 1100 (12) | 1111 1111 1000 1000 (-120) |
| 1010 1001 (-87) | 1001 1011 (-101) | 0010 0010 0101 0011 (8787) |
| 1111 1111 (-1) | 1111 1111 (-1) | 0000 0000 0000 0001 (1) |
| 0111 1111 (127) | 1000 0000 (-128) | 1100 0000 1000 0000 (-16256) |
| 0011 1111 (63) | 1110 0100 (-28) | 1111 1001 0001 1100 (-1764) |

Table 2: Summary of Functional Simulation of Carry Save Multiplier

2 Introduction

A carry-save multiplier (schematic + layout) is designed using the cells designed in assignments 1-4. In order to minimise both delay and area occupied by the layout of the CSM, the following cell sizes are used:

- **INV:** 1 ×
- **NAND:** 1 ×
- **Full Adder:** Carry-Out- 3 ×, Sum-generation- 1 ×

To simplify Layout v/s Schematic checks and make the design process modular, the CSM schematic was split into the following units that are built using the above cells:

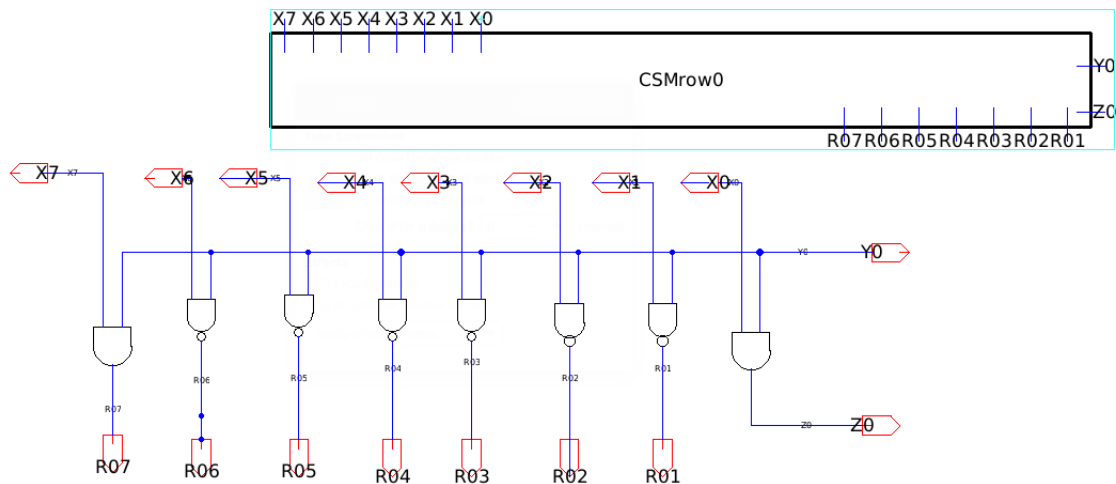


Figure 1: Row 0 of CSM

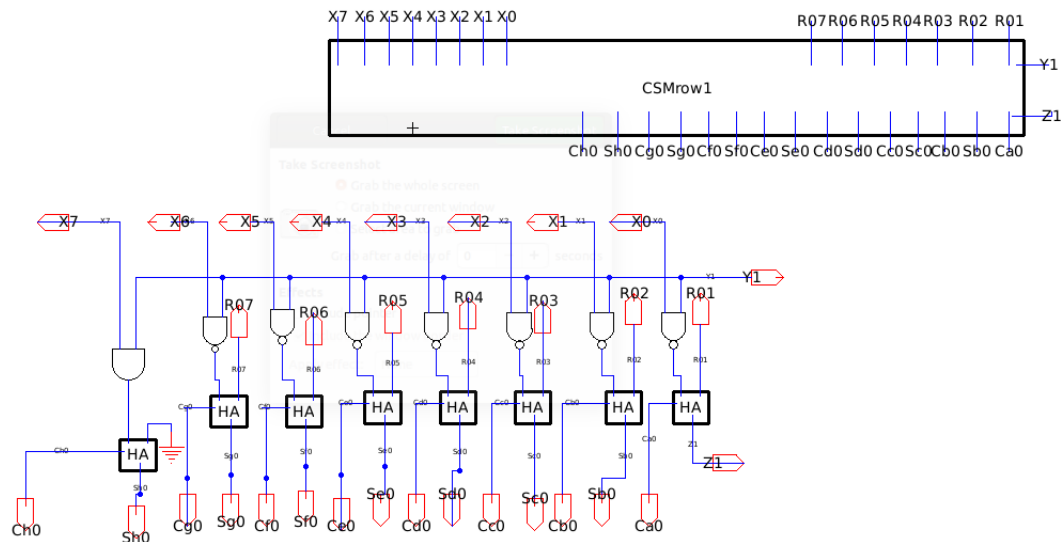


Figure 2: Row 1 of CSM

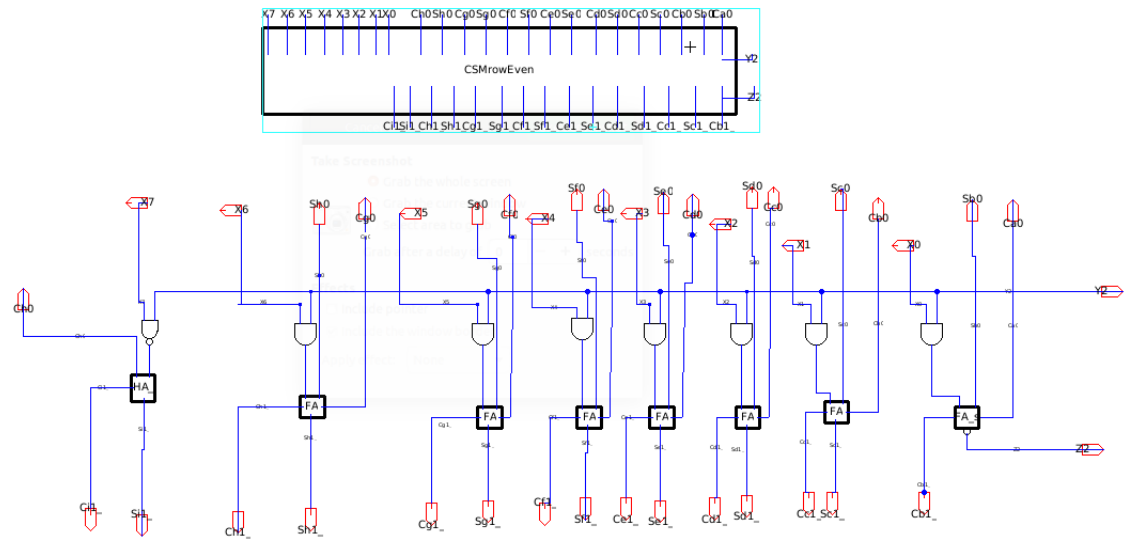


Figure 3: Rows 2, 4, 6 of CSM

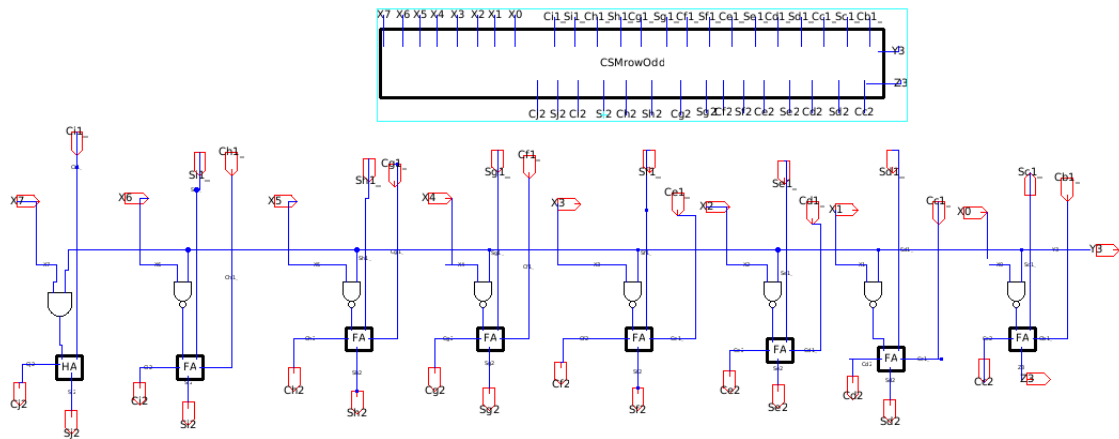


Figure 4: Rows 3 and 5 of CSM

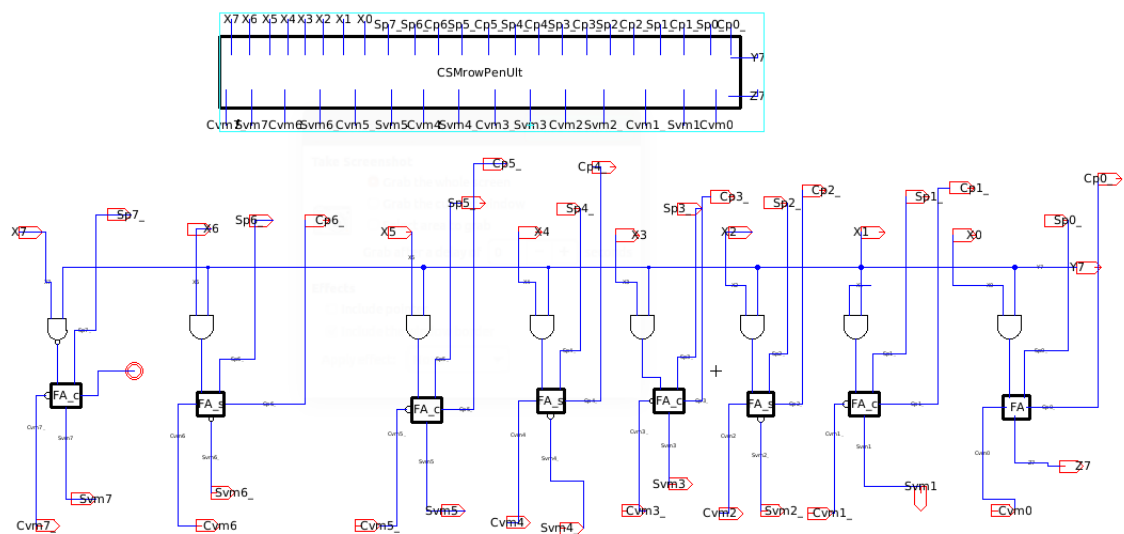


Figure 5: Row 7 (penultimate row) of CSM

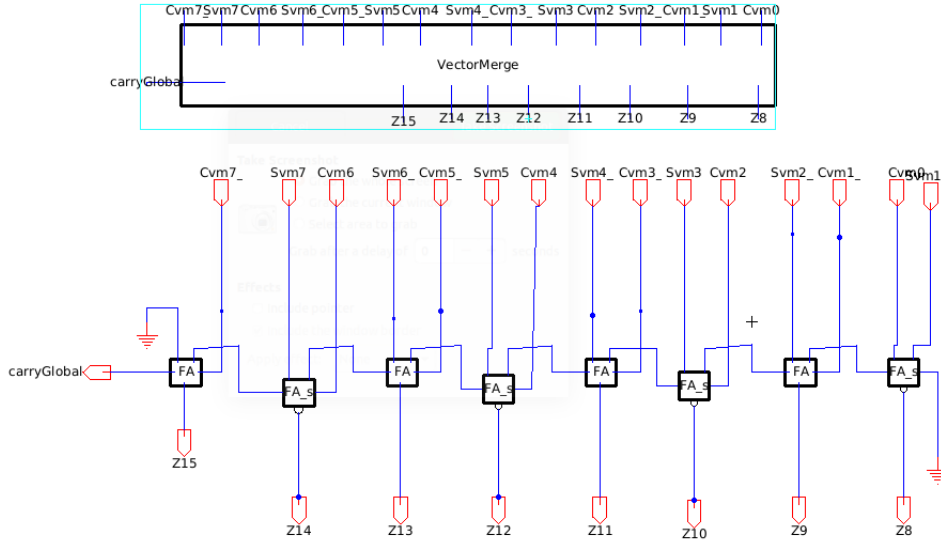


Figure 6: Ripple Carry Adder used as Vector Merge in baseline CSM

Use of Inverting Adders: Making use of the mirroring property of the components of a Full Adder circuit, every alternate array of Full Adders in the multiplier takes in inverted inputs- feeding non-inverting outputs to the next array of adders which further give out inverting outputs. This is illustrated by the schematic diagrams above- for example, the even rows take in non inverting inputs and give out inverting outputs (vice versa for odd rows). *Notation: an '_' is added to a node's name to indicate inversion.*

3 Baseline Carry Save Multiplier

3.1 Schematic

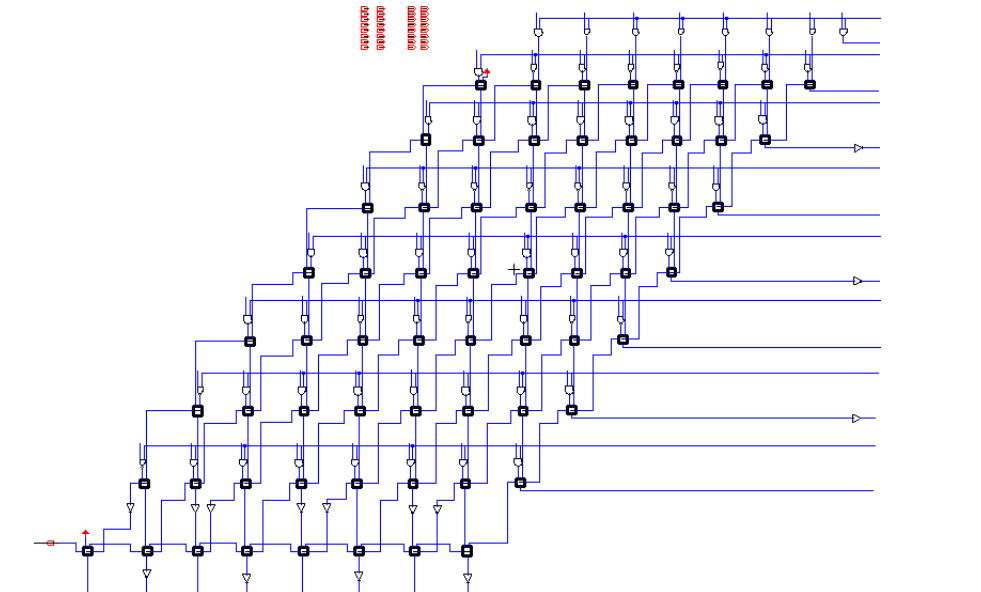


Figure 7: Schematic of CSM with Ripple Carry Adder

3.2 Layout

 


Figure 8: Layout of CSM with Ripple Carry Adder

```
Electric Messages
=====38819=====
Running DRC with area bit on, extension bit on, Mosis bit
Checking again hierarchy .... (0.004 secs)
Found 303 networks
Checking cell 'project:AND{lay}'
    No errors/warnings found
Checking cell 'project:NAND{lay}'
    No errors/warnings found
Checking cell 'project:CSMbaseline{lay}'
=====38820=====
Hierarchical NCC every cell in the design: cell 'project:CSMbaseline{sch}' cell 'project:CSMbaseline{lay}'
Comparing: project:AND{sch} with: project:AND{lay}
    exports match, topologies match, sizes not checked in 0.001 seconds.
Comparing: project:NAND{sch} with: project:NAND{lay}
    exports match, topologies match, sizes not checked in 0.001 seconds.
Comparing: project:HAdder{sch} with: project:HAdder{lay}
    exports match, topologies match, sizes not checked in 0.001 seconds.
Comparing: project:FA_SumNI{sch} with: project:FA_SumNI{lay}
    exports match, topologies match, sizes not checked in 0.001 seconds.
Comparing: project:FAdder{sch} with: project:FAdder{lay}
    exports match, topologies match, sizes not checked in 0.001 seconds.
Comparing: project:HAdder_low{sch} with: project:HAdder_low{lay}
    exports match, topologies match, sizes not checked in 0.002 seconds.
Comparing: project:FA_CountNI{sch} with: project:FA_CountNI{lay}
    exports match, topologies match, sizes not checked in 0.002 seconds.
Comparing: project:CSMbaseline{sch} with: project:CSMbaseline{lay}
    exports match, topologies match, sizes not checked in 0.011 seconds.
Summary for all cells: exports match, topologies match, sizes not checked
NCC command completed in: 0.032 seconds.
    No errors/warnings found
0 errors and 0 warnings found (took 6.11 secs)
```

Figure 9: Layout vs Schematic and Design Rule Check for complete Layout

3.3 Cells Used

3.3.1 NAND

 


Figure 10: Layout of NAND 1x cell

```
-----32-----
Running DRC with area bit on, extension bit on, Mosis bit
Checking again hierarchy .... (0.0 secs)
Found 15 networks
Checking cell 'project:NAND[lay]':
No errors/warnings found
0 errors and 0 warnings found (took 0.147 secs)
-----33-----
Hierarchical NCC every cell in the design: cell 'project:NAND[sch]' cell 'project:NAND[lay]'
Comparing: project:NAND[sch] with: project:NAND[lay]
exports match, topologies match, sizes not checked in 0.021 seconds.
Summary for all cells: exports match, topologies match, sizes not checked
NCC command completed in: 0.031 seconds.
```

Figure 11: Layout vs Schematic and Design Rule Check for NAND

3.3.2 INV

 


Figure 12: Layout of INV 1× cell

```
Hierarchical NCC every cell in the design: cell 'project:INV_1x{sch}' cell 'project:INV_1x{lay}'
Comparing: project:INV_1x{sch} with: project:INV_1x{lay}
  exports match, topologies match, sizes not checked in 0.002 seconds.
Summary for all cells: exports match, topologies match, sizes not checked
NCC command completed in: 0.003 seconds.
=====51=====
Running DRC with area bit on, extension bit on, Mosis bit
Checking again hierarchy .... (0.0 secs)
Found 11 networks
0 errors and 0 warnings found (took 0.001 secs)
```

Figure 13: Layout vs Schematic and Design Rule Check for INV

3.3.3 Full Adder

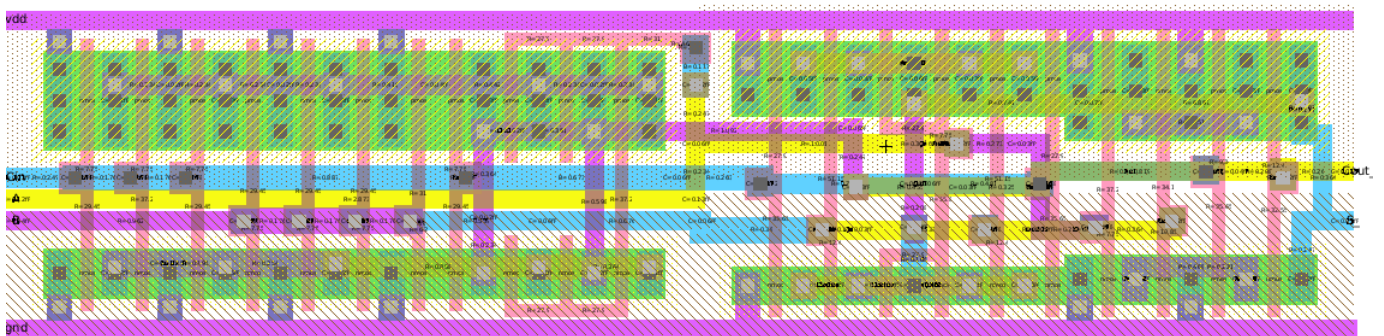


Figure 14: Layout of Full Adder 3×-1× cell

 


Figure 15: Layout vs Schematic and Design Rule Check for FA

3.4 Layout Characteristics

The layout occupies an area of $2248\lambda \times 409\lambda$, where $\lambda = 11\text{nm}$.

| Parameter | Value |
|-------------------------------|-------------------|
| Length | 2248λ |
| Width | 409λ |
| Area | $111.251 \mu m^2$ |
| Aspect Ratio | 1:5.50 |
| Propagation Delay (schematic) | 453 ps |
| Prop Delay (RC netlist) | 575.58 ps |
| Layout Efficiency | 1.271 |

Layout Characteristics for baseline Carry Save Multiplier

3.5 Functional Simulation

3.5.1 63×-28

 


Figure 16: $X = 0011\ 1111$, $Y = 1110\ 0100$, $Z = 1111\ 1001\ 0001\ 1100$

3.5.2 127×-128

 


Figure 17: X = 0111 1111, Y = 1000 0000, Z = 1100 0000 1000 0000

3.5.3 9×15

 


Figure 18: X = 0000 1001, Y = 0000 1111, Z = 0000 0000 1000 0111

3.5.4 -10×12

 


Figure 19: X = 1111 0110, Y = 0000 1100, Z = 1111 1111 1000 1000

3.5.5 -87×-101

 


Figure 20: X = 1010 1001, Y = 1001 1011, Z = 0010 0010 0101 0011

4 Pipelined CSM

4.1 Flip-Flop Circuit

A C^2MOS Flip-Flop was designed with sizes chosen appropriately to minimize the setup and clock-to-q delays.

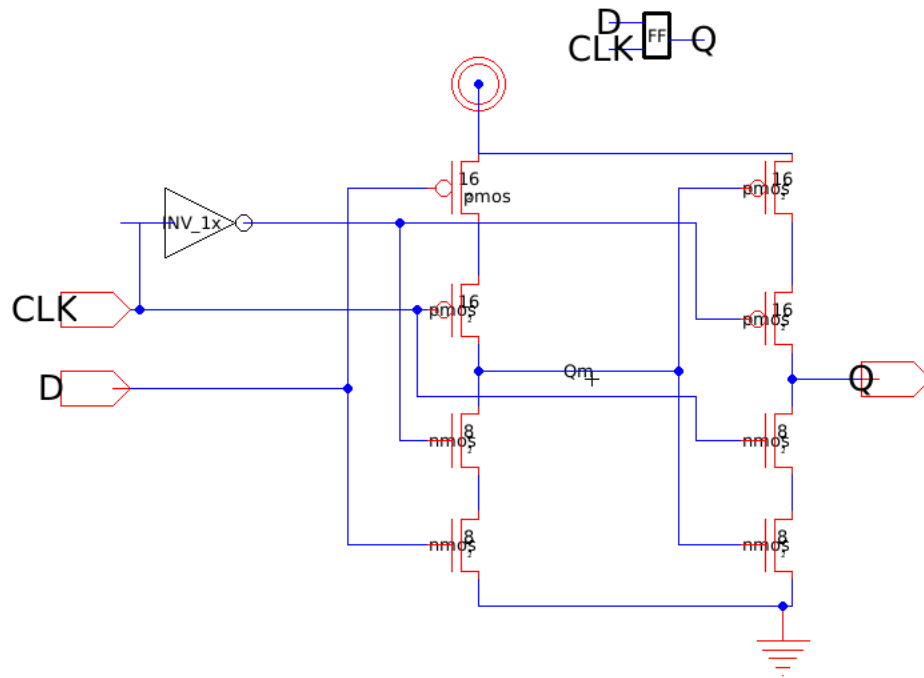


Figure 21: C2MOS Flop

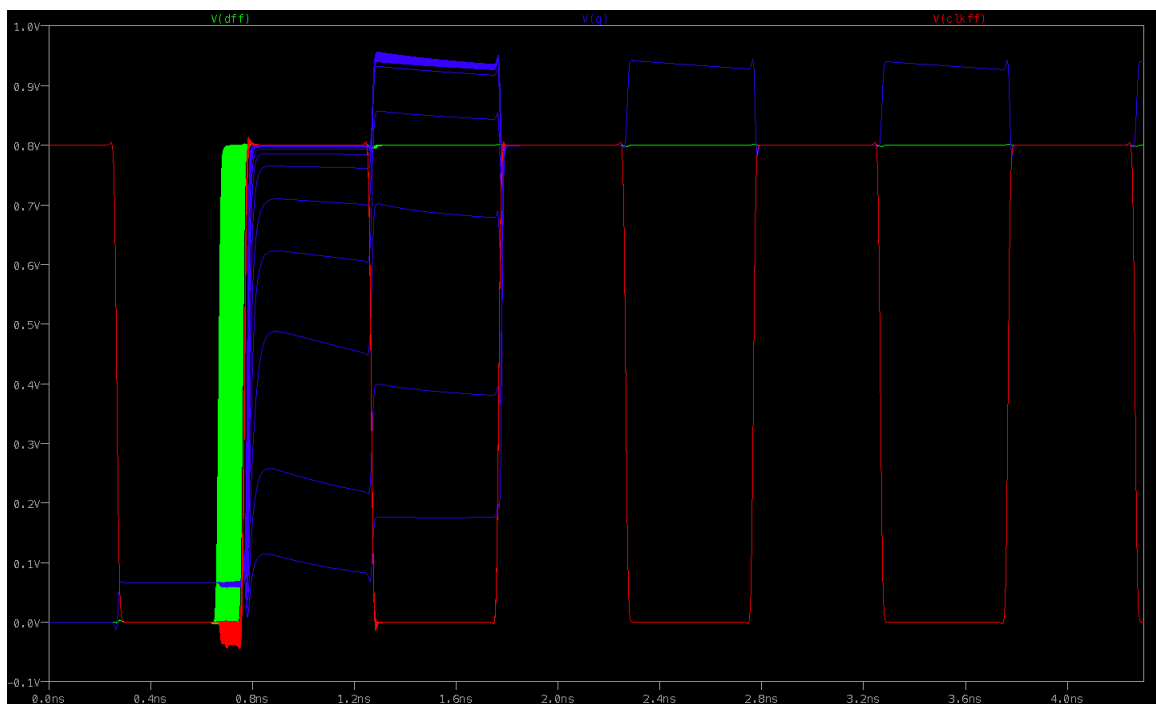


Figure 22: Functional Simulation of Flip Flop



Figure 23: T_{dq} v/s T_{dc} of Flip-Flop

From the graph and results tabulated, the minimum T_{dq} is 43ps which occurs at T_{dc} of 9.3ps. Therefore, propagation delay when using this Flip Flop is 43 ps and the setup time is 9.3 ps.

4.2 Pipelining

An array of Flip-Flops were placed between rows 5 and 6 of the schematic to store the state of the computation. This enable the circuit to operate at a time period that is equal to $\min\{\text{Input} \rightarrow \text{Pipeline Array delay}, \text{Pipeline Array} \rightarrow \text{Output Delay}\}$. To maximize the operating frequency, the array is placed midway- this was done by identifying the node in the critical model that was equally far in terms of delay from the input and the output.

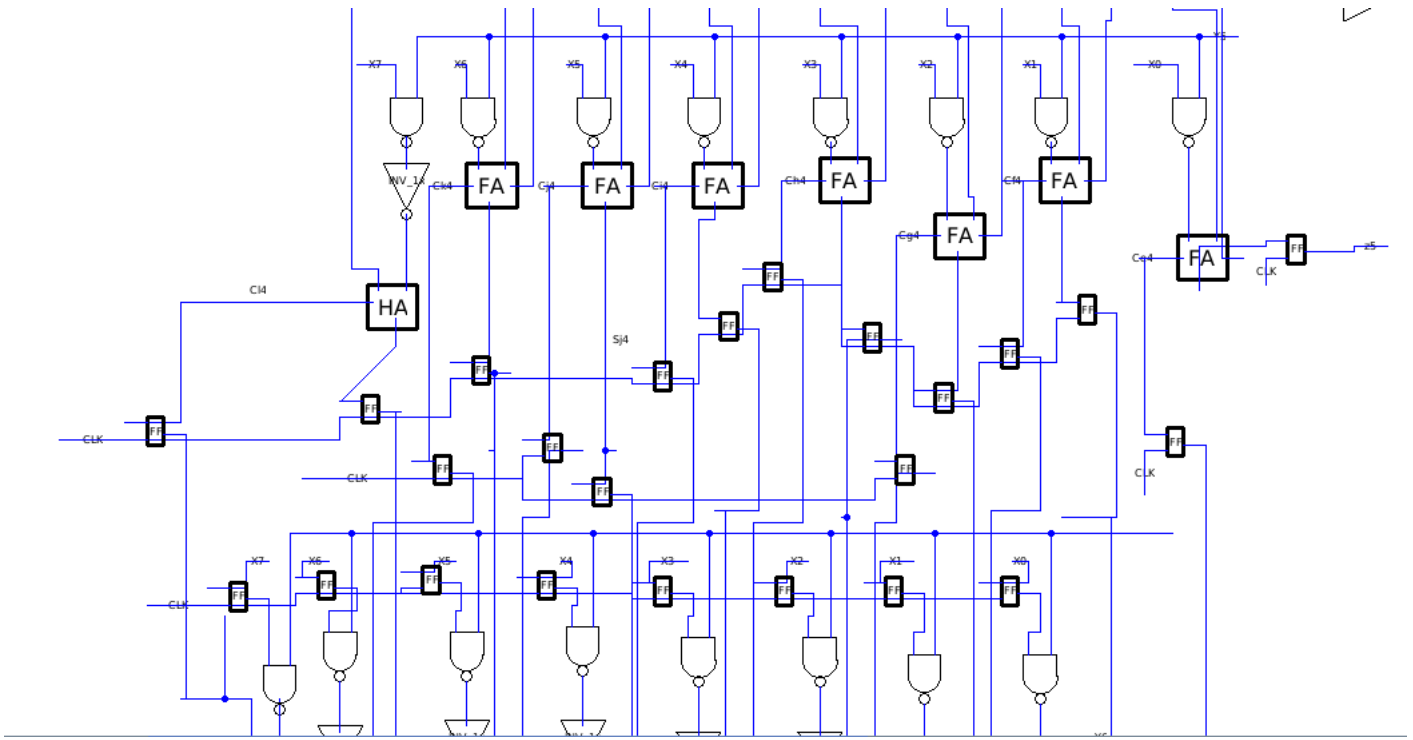


Figure 24: Location of Pipeline FF array in the schematic

4.2.1 Minimum Operating Period

The following table lists the operating delay for pipelined and non-pipelined versions of the circuit. Hence, pipelining enables a speedup of about $1.79\times$.

| CARRY SAVE MULTIPLIER | NON-PIPELINED | PIPELINED |
|-----------------------|-----------------------|-----------------------|
| Schematic Netlist | 485 ps (2.062 GHz) | 270 ps (3.704GHz) |
| Layout Netlist | 610 ps (1.639 GHz) | 382 ps (2.618 GHz) |

4.3 Functional Simulation

4.3.1 -1×-1

 


Figure 25: X = 1111 1111, Y = 1111 1111, Z = 0000 0000 0000 0001

4.3.2 -11×-11 with input setup and output capture flops

 


Figure 26: $X = 1111\ 0101$, $Y = 1110\ 0101$, $Z = 0000\ 0000\ 0111\ 1001$

5 Alternate Vector Merge Adders

5.1 Carry Skip Adder

Two versions of Carry Skip Adder were tried- $N = 4$ and $N = 2$. The $N = 4$ version gave a performance benefit for the input sequence that triggers the critical path (-1×-1), while $N = 2$ did not. This is because the net delay due to the MUX and XOR gates is significant in the $N = 2$ version.

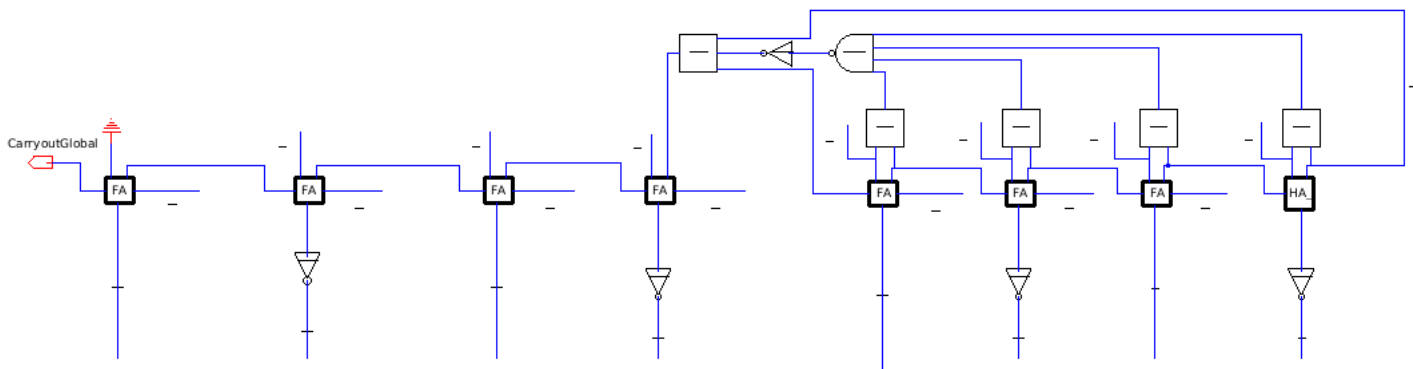


Figure 27: Carry Skip Adder Schematic used in place of Ripple Adder in the Vector Merge Stage

5.1.1 Delay Comparison

Comparison of propagation delays for the Carry-Save Multiplier by using Carry Skip adder.

| | CRITICAL DELAY MEAS. | |
|--------------|-----------------------------|----------------|
| NETLIST USED | SCHEME | CRITICAL DELAY |
| SCHEMATIC | CARRY SAVE MULTIPLIER | 417 ps |
| SCHEMATIC | CARRY SKIP MULTIPLIER (N=4) | 420 ps |
| SCHEMATIC | CARRY SKIP MULTIPLIER (N=2) | 442 ps |

5.2 Carry Lookahead Adder

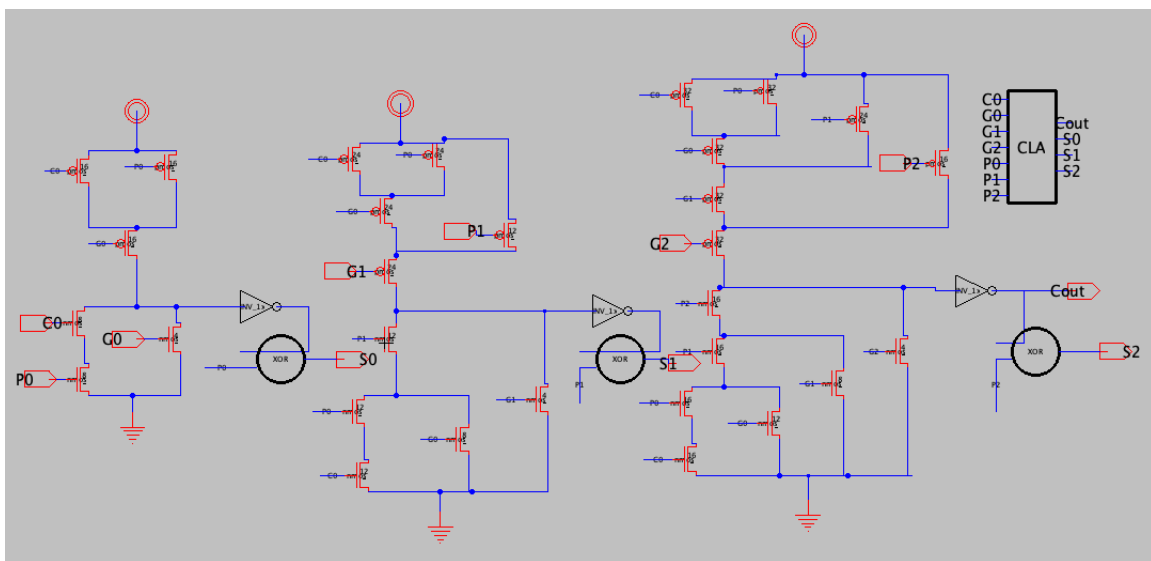


Figure 28: Carry Lookahead Adder Schematic

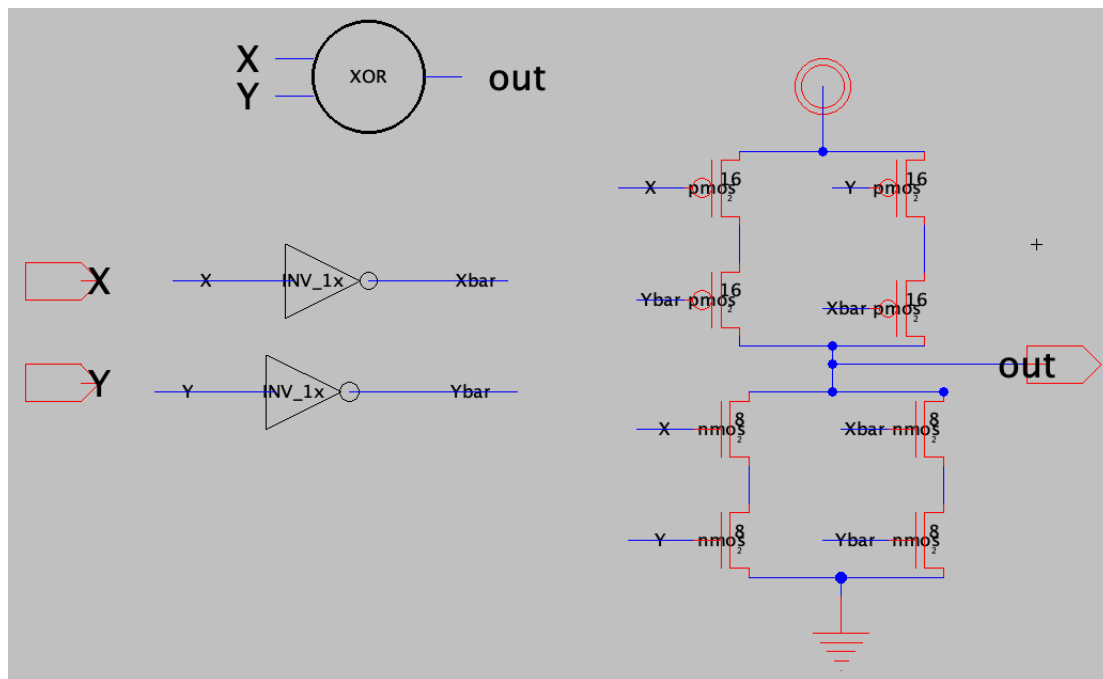


Figure 29: XOR gate used in the Carry Lookahead Adder

 


Figure 30: Carry Lookahead Adder used in Vector Merge Stage

5.2.1 -1×1 with 3% decrease

 


Figure 31: $X = 1111\ 1111$, $Y = 1111\ 1111$, $Z = 0000\ 0000\ 0000\ 0001$

Using carry look ahead adder decreases the delay. The decrease in delay however depends on the input and varies from about 3-30%. Other inputs such as -11×11 have a 30% decrease in delay(reduced to 280ps from 400ps).

★ ★ ★